

第一次期中考解答

第一題

A.



B.

C.

D.

第二題

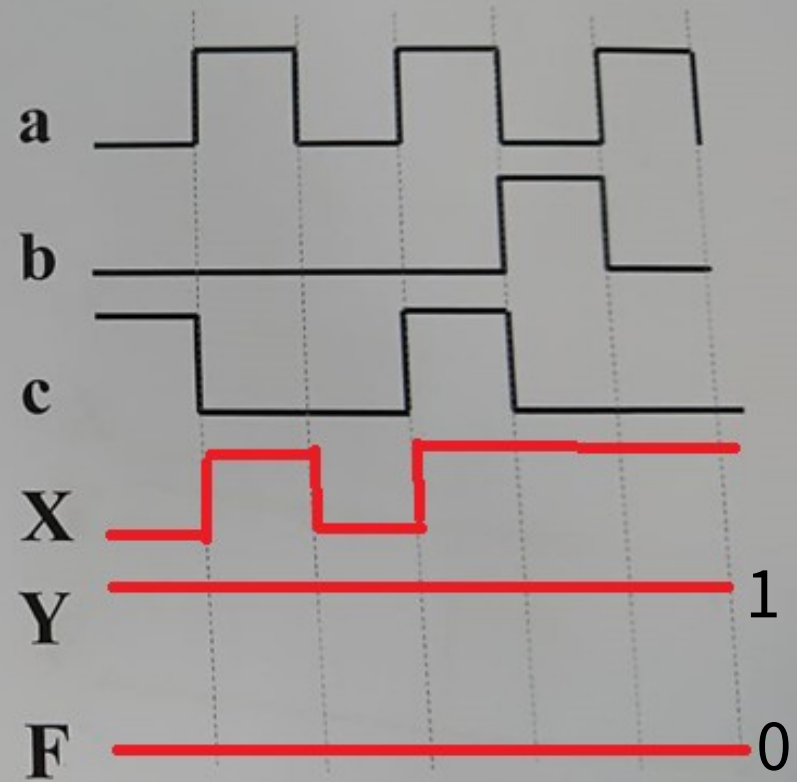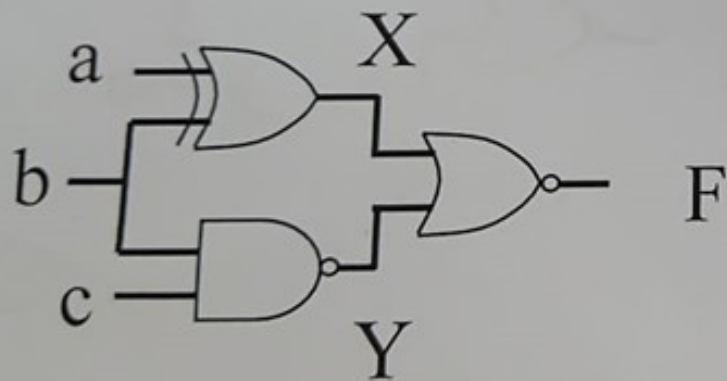2. Please draw the time diagram to show the responses (X, Y, F) of the three gates.
(9%)



第三題

Please prove $(x + y + z)' = x' \cdot y' \cdot z'$ and $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$

x	y	z	$(x + y + z)'$	$x' \cdot y' \cdot z'$	$x \cdot (y + z)$	$(x \cdot y) + (x \cdot z)$
0	0	0	1	1	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	0	0	0
1	0	1	0	0	1	1
1	1	0	0	0	1	1
1	1	1	0	0	1	1

第四題

選項 E 沒有兩個都寫會扣分

A.Power dissipation：功率消耗，元件上會耗散能量造成輸出與輸入之功率有差額

B.Fan-out 一個 logic gate：可驅動同類 logic gate 的數量

C.Gate propagation delay：訊號從輸入穩定到可接收穩定輸出的時間

D.Gray code vs. binary：code gray code 一次只翻轉 1bit，較 binary code 省電

E.Advantages of 2' s complement representation：

1、沒有正負 0

2、加減法皆只需使用加法器，電路設計上較簡單

F.A/D converter：將類比訊號轉換至數位訊號的儀器

第五題

沒化簡扣部分分數

(A)

ab \ cd	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	0	0	1	1
10	0	0	0	1

$$F = (b+d') (a+d' +c)$$

5. The truth table for functions F is listed as:

(a) Simply F with K-map and implement it with product of sums (5%)

(b) Simply F with K-map and implement it with sum-of-products (5%)

a	b	c	d	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

第五題

沒化簡扣部分分數

(B)

ab \ cd	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	0	0	1	1
10	0	0	0	1

$$F = cd' + a'd' + abc$$

5. The truth table for functions F is listed as:

(a) Simplify F with K-map and implement it with product of sums (5%)

(b) Simplify F with K-map and implement it with sum-of-products (5%)

a	b	c	d	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

第六題

6. Simply function F with K-map and draw the NOR logic diagram of it. (10%)

$$F(A,B,C,D)=A'BC'+ABC'+CD+A'B'CD'$$

AB \ CD	00	01	11	10
00	0	0	1	1
01	1	1	1	0
11	1	1	1	0
10	0	0	1	0

沒化簡扣部分分數，Kmap 錯全錯


做 Kmap(答案不只一種)

$$= ((B' + C' + D)' + (A' + C' + D)' + (B + C)'$$

第六題

6. Simply function F with K-map and draw the NOR logic diagram of it. (10%)

$$F(A,B,C,D)=A'BC'+ABC'+CD+A'B'CD'$$

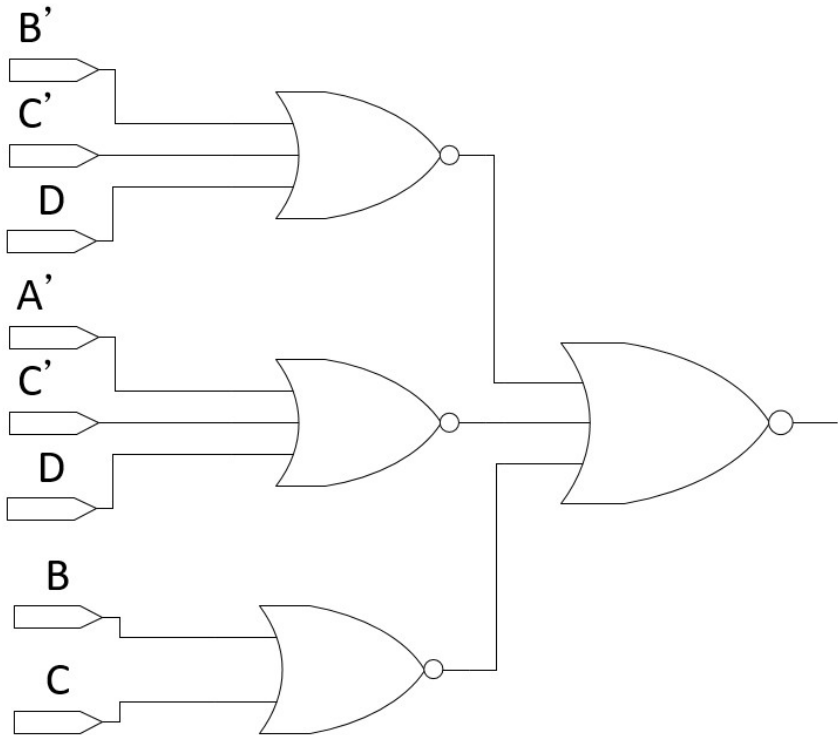

第七題

7. Simply function F with K-map and draw the NAND logic diagram of it. (10%)

$$F(A,B,C,D)=A'B'D'+ABD'+AC'D+BCD'$$


AB \ CD	00	01	11	10
00	1	0	0	1
01	0	0	0	1
11	1	1	0	1
10	0	1	0	0

沒化簡扣部分分數，Kmap 錯全錯

做 Kmap (答案不只一種)

$$(F) = ((A' B' D')' (ABC')' (AC' D)' (BCD')')'$$

第七題

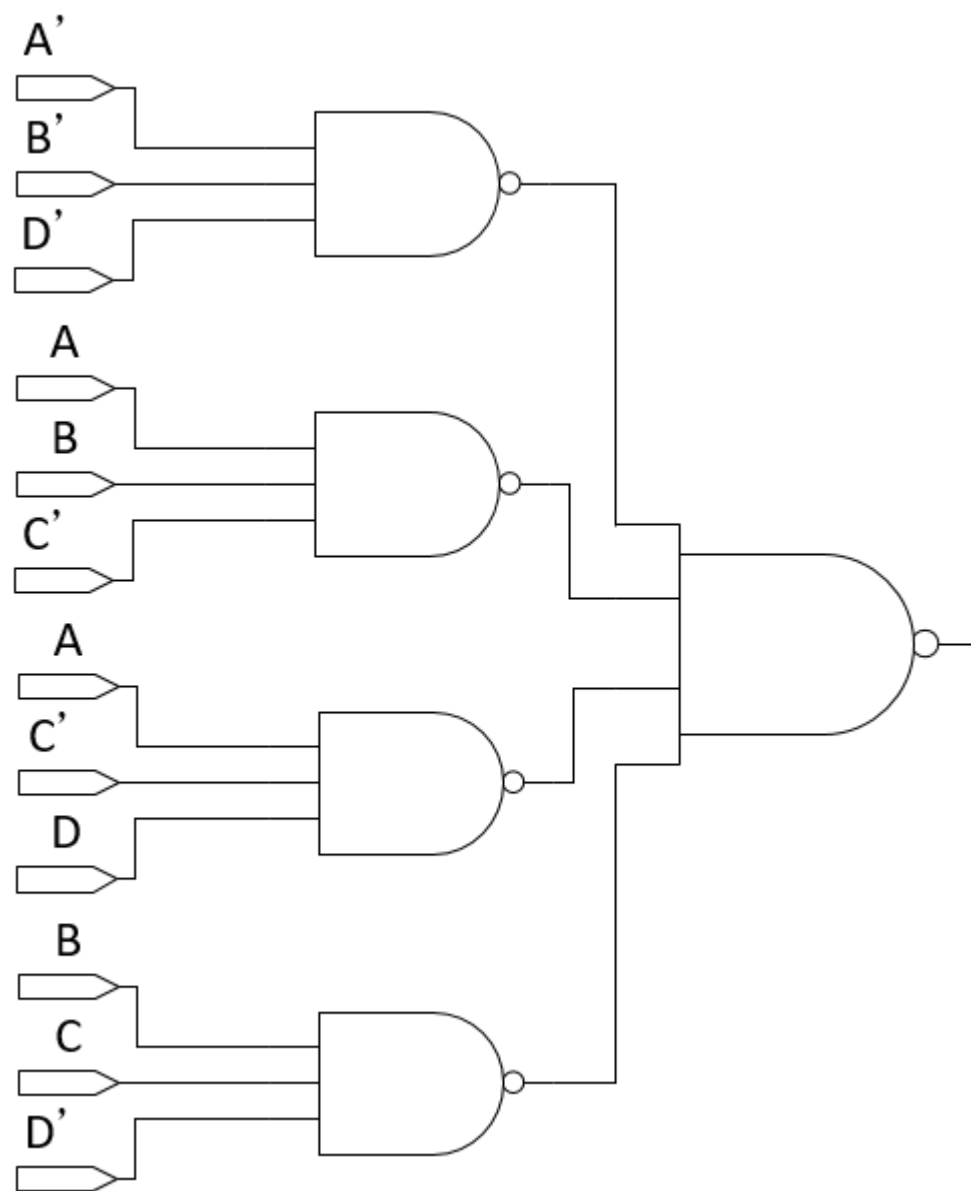

第八題

8. Simply the following function with K-map and implement it with sum-of-products (8%) and product-of-sums (8%).

$F(A,B,C,D) = \Sigma (0,6,7,8,14,15)$ with don't care condition $d(A,B,C,D) = \Sigma (2,4,10)$

Sum-of-products

AB \ CD	00	01	11	10
00	1	0	0	X
01	X	0	1	1
11	0	0	1	1
10	1	0	0	X

沒化簡扣部分分數

$$F = BC + B' D'$$

第八題

8. Simply the following function with K-map and implement it with sum-of-products (8%) and product-of-sums (8%).

$F(A,B,C,D) = \Sigma (0,6,7,8,14,15)$ with don't care condition $d(A,B,C,D) = \Sigma (2,4,10)$

Product-of-sum

AB \ CD	00	01	11	10
00	1	0	0	X
01	X	0	1	1
11	0	0	1	1
10	1	0	0	X

沒化簡扣部分分數

$$F = (B' + C)(B + D')$$